
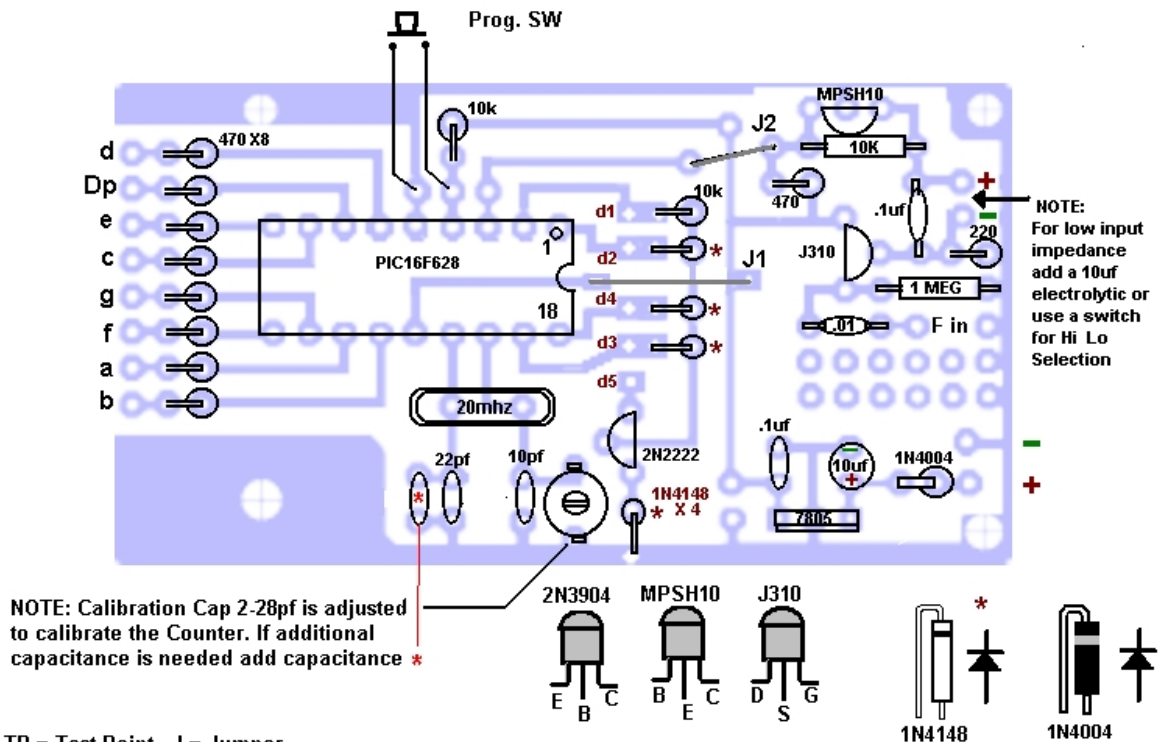


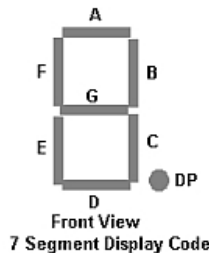


DL4YHF Frequency Counter Parts Overlay W/ XRAY View of PCB Pattern



WARNING! Do not install 20Mhz Crystal or Pic Microcontroller until you check the 5vdc Supply. There should be 5vdc at Pin 4 and Pin 14 only check all other pins to verify that they are clear



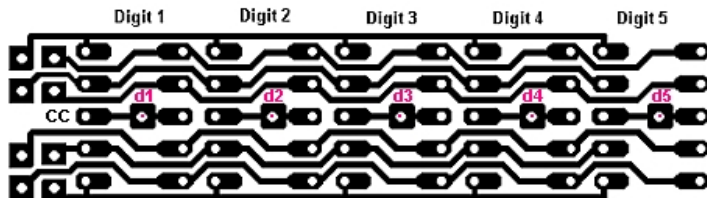
The 7 Segment Displays are Common Cathode
0.39" high characters



The Frequency Counter has to have some kind of buffered input to the PIC16F628. The low impedance input on DL4YHF's website can be used. I used a 2N2222 for that circuit it worked great for audio frequency readout. The high impedance input is used on the HF frequency input and is more stable. The 20db gain preamplifier circuit was used on a Swan 350D to tap the VFO frequency with good results.

I have not built the Prescaler shown below, I have found many circuits but most of the ICs used are obsolete, this circuit uses a currently available IC that is a surface mount device MC 12080D Jameco Electronics PN # 867780 and also a SOIC board to mount the SMD device on PN# 207360. I added the variable capacitor to allow for adjusting the output frequency. The final adjustment should be made after the Counter is installed to allow for the capacitance of the shielded cable. When this counter is used on the HF bands or a communications receiver you have to reprogram the counter to add or subtract the selected VFO or IF frequency. Example for 80 and 40 meters you subtract the desired frequency for 20, 15 10 meters you add the frequency. This has to be done with the program switch. It should take 10 seconds or less to add or subtract the frequency once you get used to the program.

20db gain 30MHz bandwidth preamplifier.

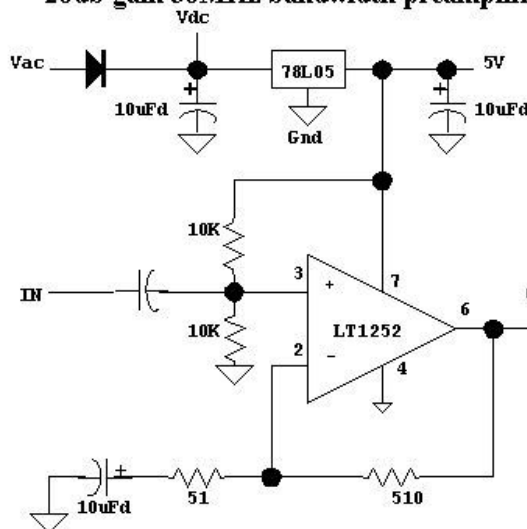

IN capacitor would typically be in the order of 5pf to 100pf.


(As small as possible while providing sufficient coupling)

01 is OK if signal is taken from a buffered signal source.

OUT capacitor would be on the order of 100pf depending on type of cable used to carry signal to counter.


The LT1252 CN8 is available from Linear Technologies

High Impedance Input Circuit

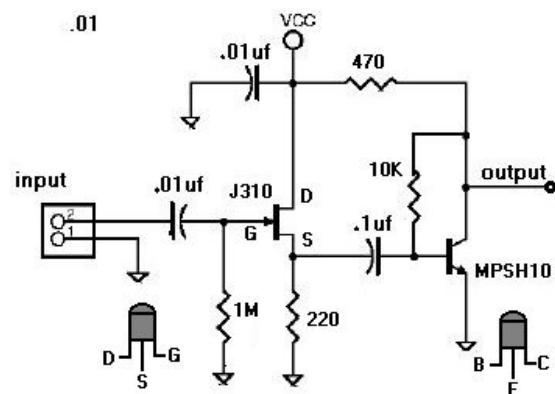


Prescaler Circuit

The MC12080 is a SMT device

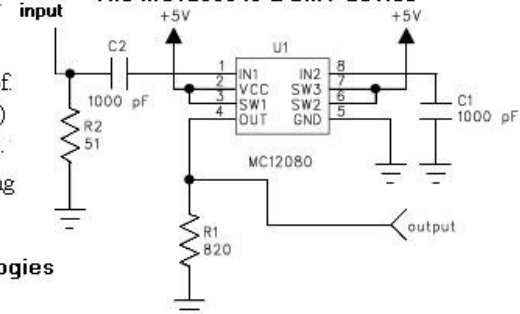

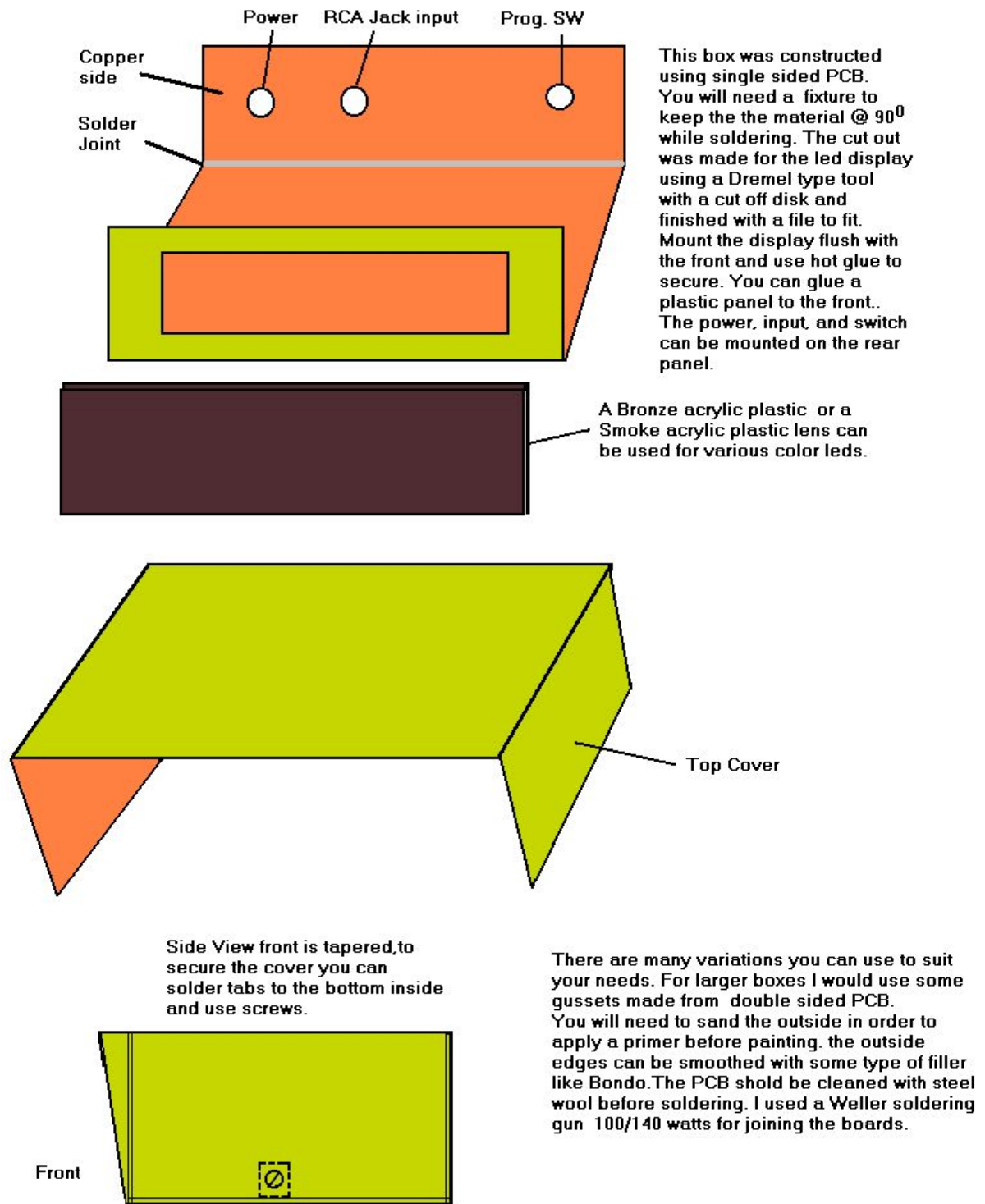Construction of a PCB project box for the Freq. Counter



2Er0	Select to read direct freq. input	Quit	Quit without saving anything
TABLE	Select and hold TABLE will flash on and off, release switch press once to select freq. in table. when the freq. is displayed press switch and hold release and goto Add or Sub and hold to save that freq.	Add	To Add TABLE Freq.
45500		Sub	To Subtract TABLE Freq.
50000		NoPSL	No Power Saver feature
41943		PSALE	Power Saver feature
44336			
10700			

The Program switch is a momentary N/O switch